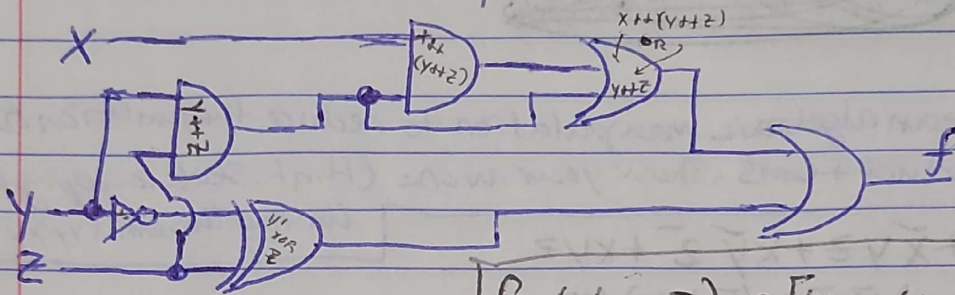


Lab 1: Combinational Logic: Simulation + Design

1. Using ~~the~~^a logic simulator, either the one embedded in Section 1.4.3 of the interactive text book or the one available at <https://simulator.io/board>, determine the function f implemented by the circuit in this figure



$$f = (Y' \text{ XOR } Z) \text{ OR } [(X \text{ AND } (Y \text{ AND } Z)) \text{ OR } (Y \text{ AND } Z)]$$

a) Show the truth table

X	Y	Z	Y'	Y AND Z	Y' XOR Z	X AND (Y AND Z)	(X AND (Y AND Z)) OR (Y AND Z)	(Y' XOR Z) OR [(X AND (Y AND Z)) OR (Y AND Z)]
0	0	0	1	0	1	0	0	1
0	0	1	1	0	0	0	0	0
0	1	0	0	0	0	0	0	0
0	1	1	0	1	1	0	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	1	1	1	1	1

Inputs Output

$$f = (Y' \text{ XOR } Z) \text{ OR } [(X \text{ AND } (Y \text{ AND } Z)) \text{ OR } (Y \text{ AND } Z)]$$

FINAL TRUTH TABLE w/ f + inputs

X	Y	Z	f = (Y' XOR Z) OR [(X AND (Y AND Z)) OR (Y AND Z)]
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Inputs Output

b. Write down the SOP (Sum-Of-Products) of the function.

$$\bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ \Rightarrow$$

$$F = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ$$

~~$$F = \bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ$$~~
~~$$F = \bar{X}(\bar{Y}\bar{Z} + YZ) + X(\bar{Y}\bar{Z} + YZ)$$~~
~~$$F = \bar{X}(Y \oplus Z) + X(Y \oplus Z)$$~~
~~$$F = (\bar{X} + X)(Y \oplus Z)$$~~
~~$$F = Y \oplus Z$$~~

c) Use Boolean algebraic manipulation to reduce the function to two product terms. Show your work (Hint: seek to apply the Uniting theorem: $XY + XY' = X$)

$$\bar{X}\bar{Y}\bar{Z} + \bar{X}YZ + X\bar{Y}\bar{Z} + XYZ$$

$$\Rightarrow (\bar{X} + X)\bar{Y}\bar{Z} + (\bar{X} + X)YZ$$

$$\Rightarrow (\text{applying the Uniting theorem}) \Rightarrow F = \bar{Y}\bar{Z} + YZ$$

2. Realize the function from part 1c in terms of only the following gates: 2-input OR, AND, NOR, NAND, and INV. (No XORs can be used). Use as few gates as possible. (Each inverter is counted as a gate. Hint: seek to apply De Morgan's laws). Using the simulator, prove the equivalence of your new circuit to the original circuit.

$$YZ + Y'Z'$$

(5 gates)

$$\text{De Morgan's: } Y'Z' = (Y+Z)'$$

$$\Rightarrow YZ + (Y+Z)'$$

(4 gates) (3 gates) • AND • OR • NOR

Y	Z	F
0	0	1
0	1	0
1	0	0
1	1	1

• X variable doesn't affect output and it is shown that the truth table from 1a is repeated twice as Y + Z change

Circuit Diagram for Lab 1

Top Circuit: Question 1 – Original Circuit

Bottom Circuit: Question 2 – New Equivalence-Original Circuit

